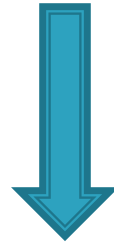


REACTANCE IN AN A.C. CIRCUIT



Combined effect of R,L and C

REACTANCE IN SERIES

- ▶ Application of Ohm's law for D.C. Circuits
- ▶ Application of Ohm's law for A.C. Circuits

Peak Voltage



Peak Current

R.M.S. Voltage



R.M.S. Current

Resistive
Circuits




I and V are in
phase

Capacitive
and
Inductive
Circuits





I and V are 90°
out of phase

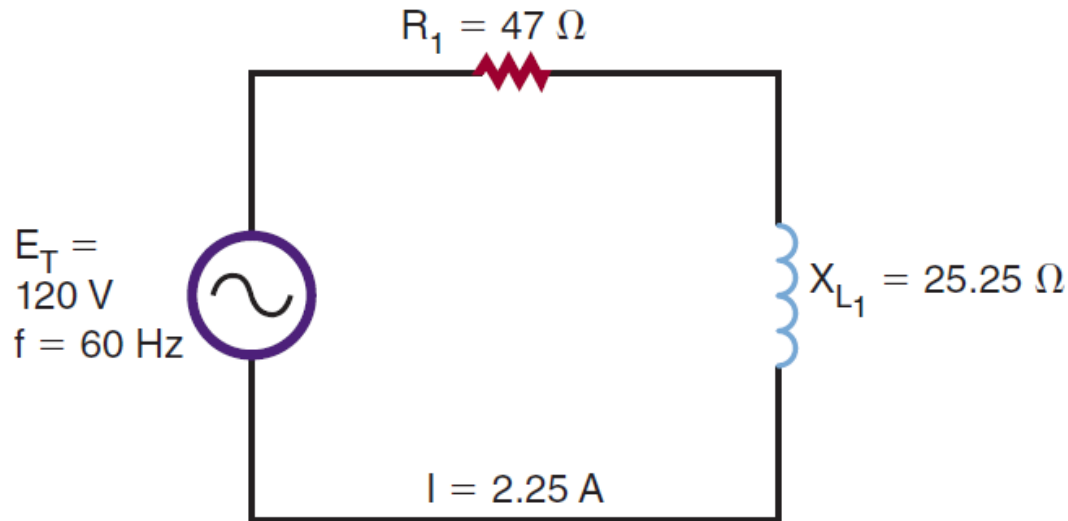COMBINATION OF REACTIVE AND RESISTIVE COMPONENTS




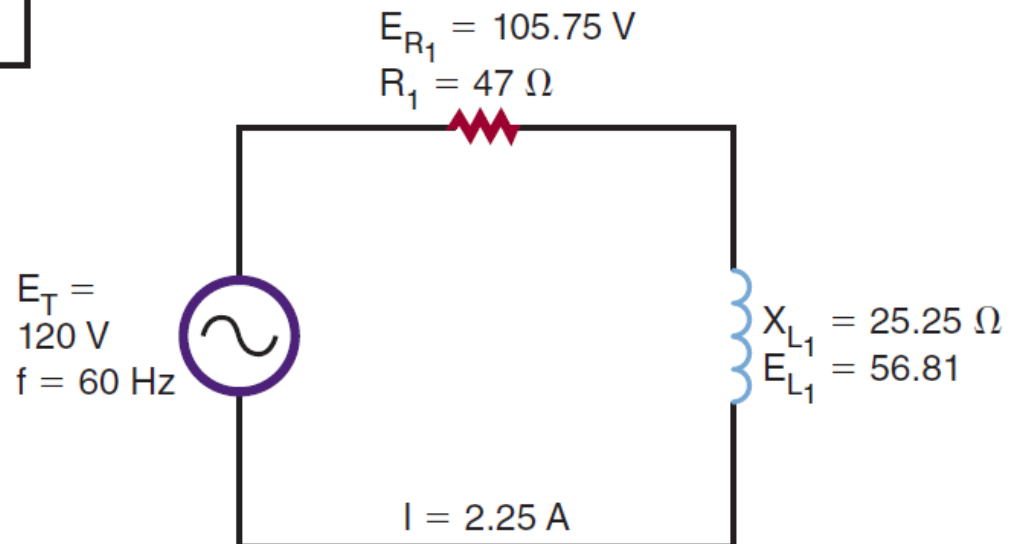Find Voltage at
each component
using Ohm's Law



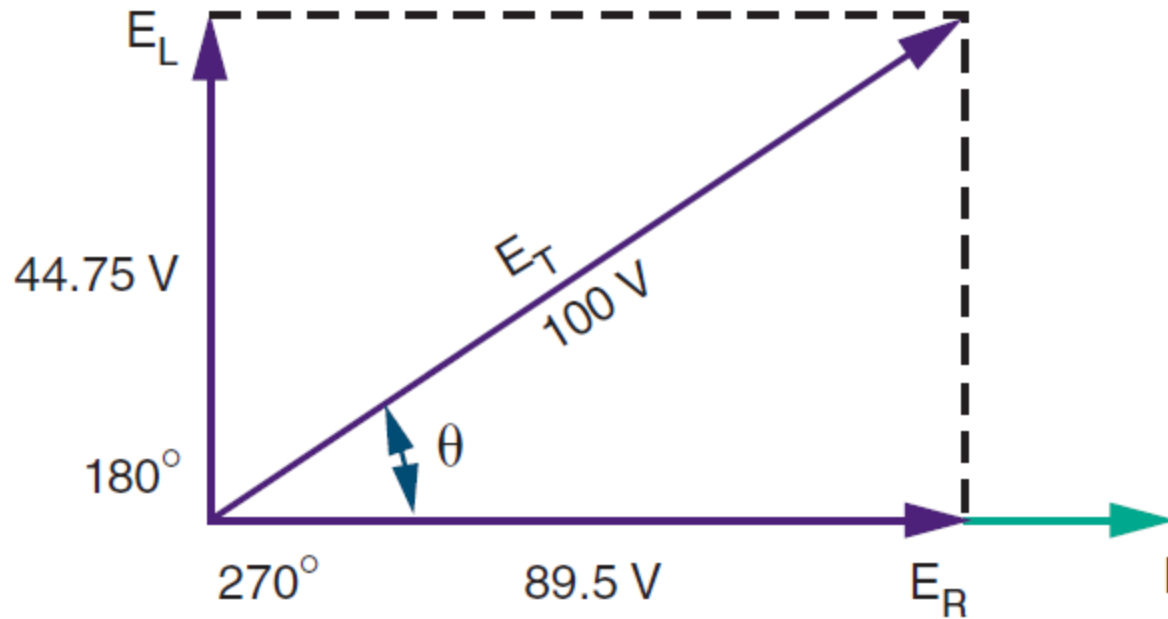

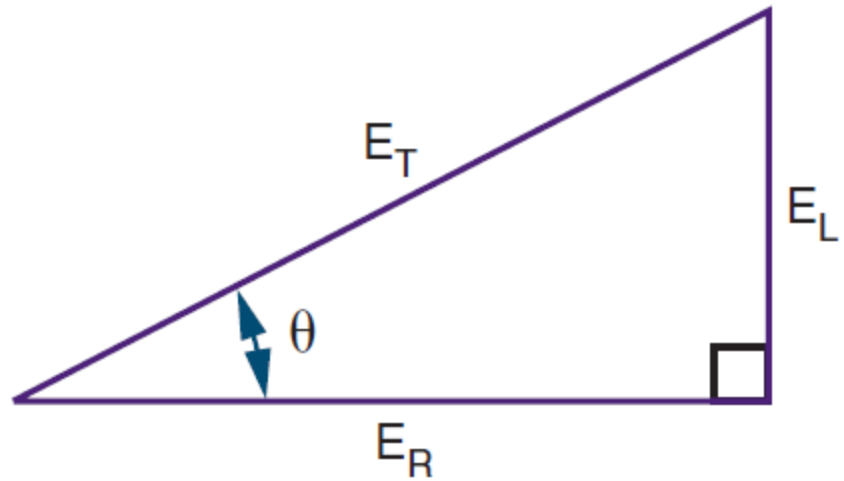- ▶ Length of arrow indicates the magnitude



The angle of the Vector $E_T(\theta)$ indicates the phase between the source voltage and current

From Pythagoras theorem,


$$E_T = \sqrt{E_R^2 + E_L^2}$$

$$\sin\theta = E_L/E_T$$


$$\cos\theta = E_R/E_T$$

$$\tan\theta = E_L/E_R$$

TIPS TO REMEMBER:

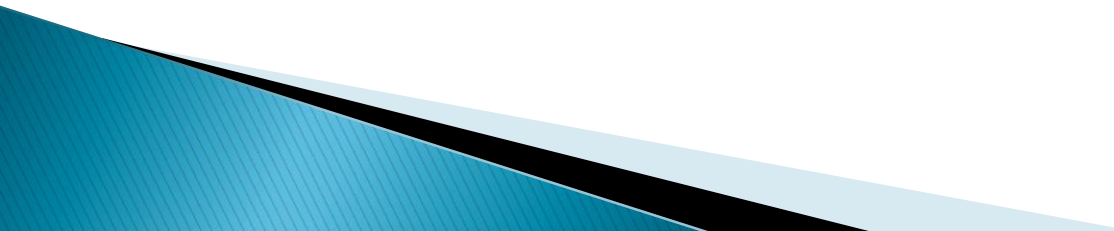
1. When Circuit is purely resistive, phase angle is 0 because V and I are in phase.
 2. As X_L increases, phase angle becomes greater
 3. At 45° , R and X_L are equal in value
 4. When a circuit contains pure inductive reactance with no resistance, phase angle increases to 90°
 5. I is same in a series circuit
- 

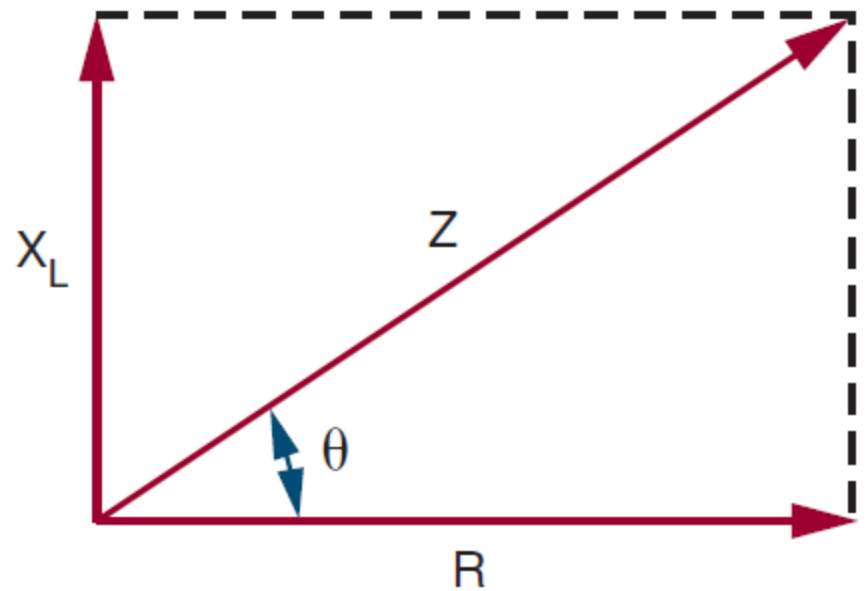1. Voltage drop is directly proportional to R or X of that component
2. So, we can have X and R vectors proportional to voltage vectors




The combined effect of R and X is called as IMPEDANCE(Z)


SERIES RC CIRCUIT

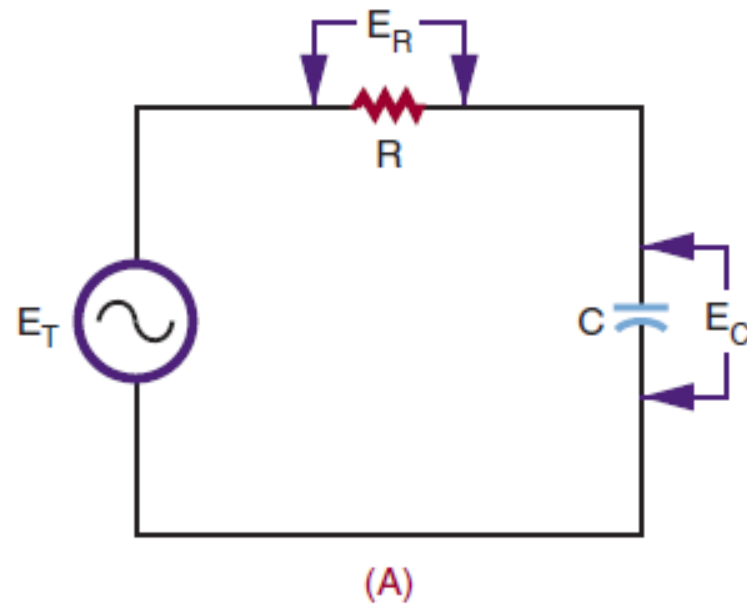

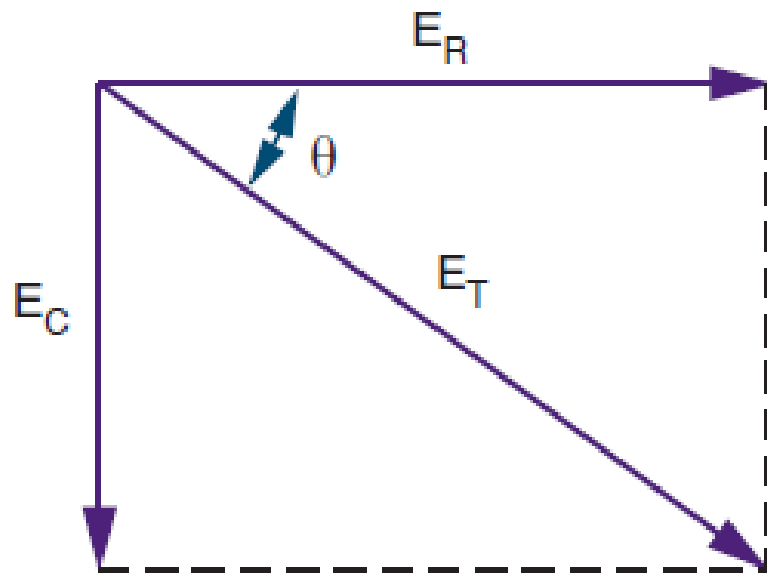Draw Voltage Vectors and Resistance vectors




(B)


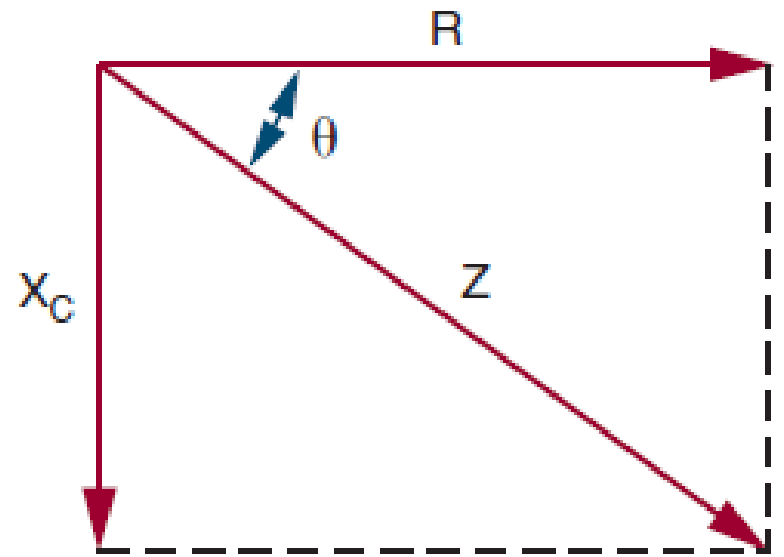


(C)

REACTANCE IN PARALLEL CIRCUIT

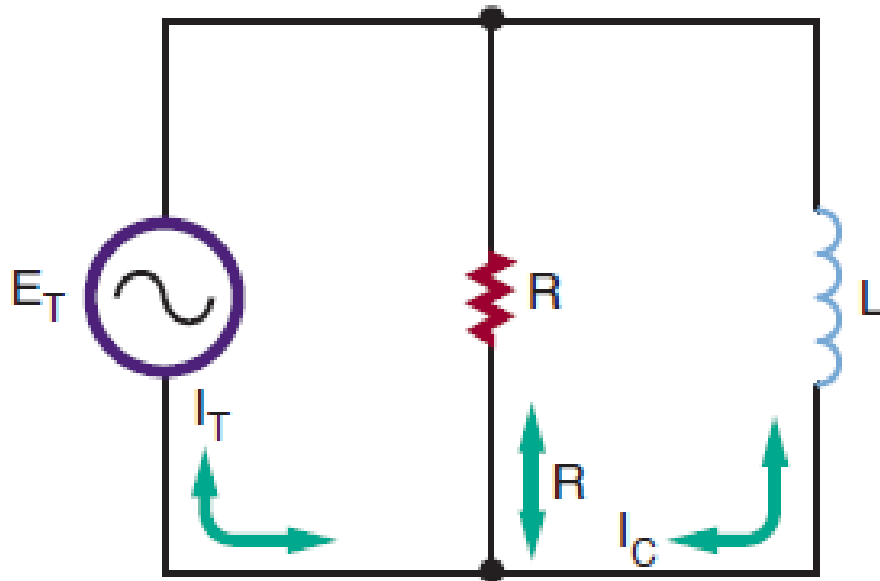- ▶ Voltage in Parallel components is same




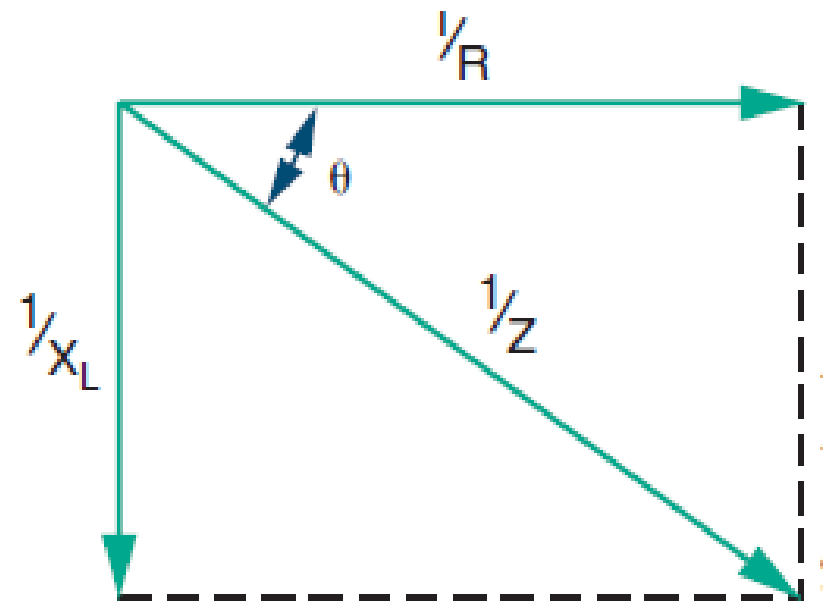
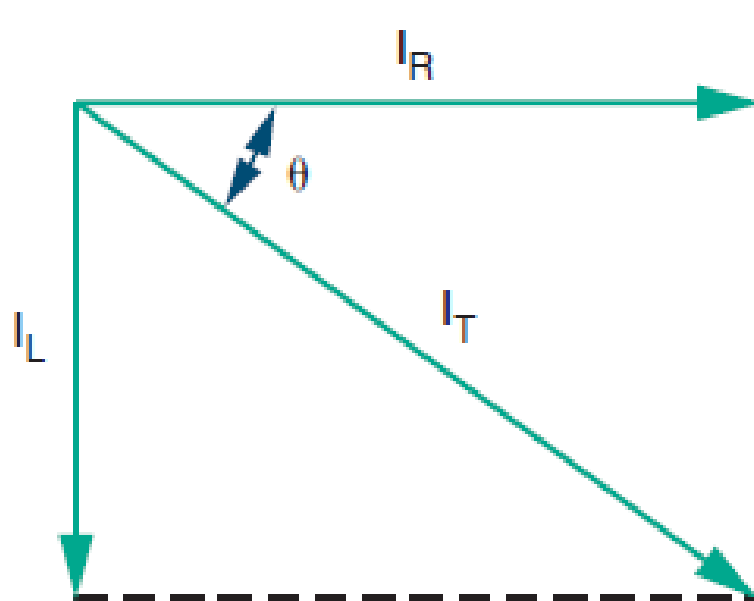


$$I = \sqrt{I_R^2 + I_L^2}$$

$$1/Z = 1/R + 1/X_L \angle 90$$

REACTANCE IN PARALLEL CIRCUIT

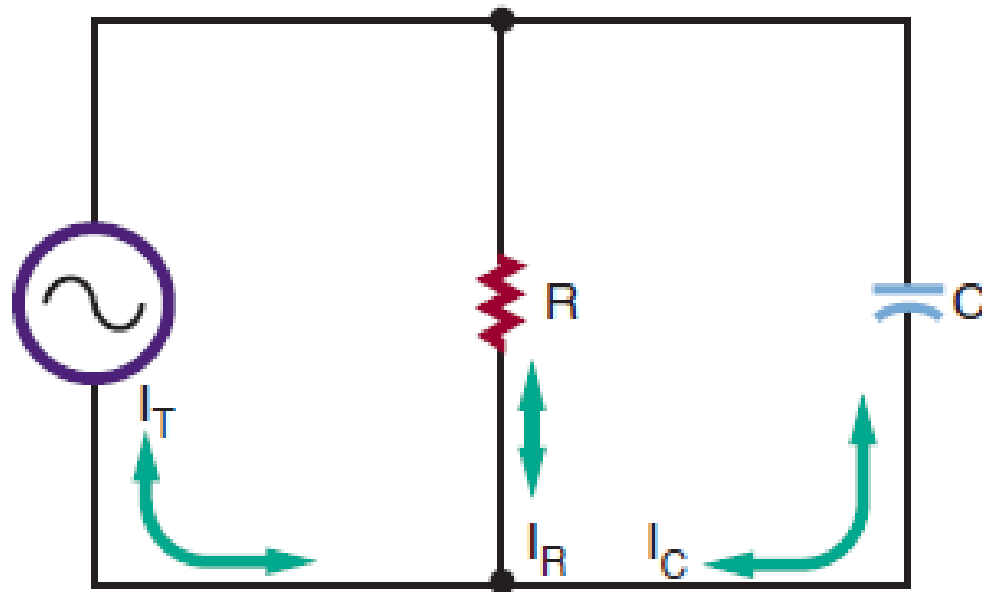


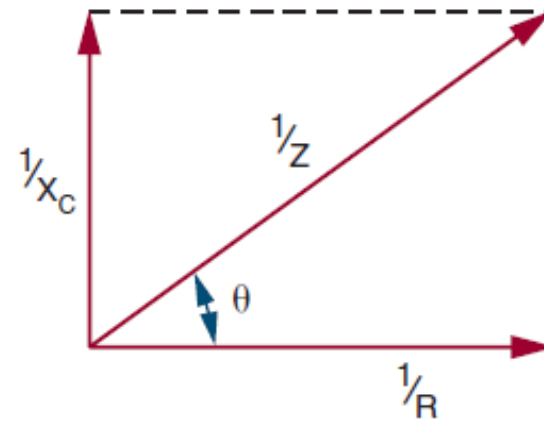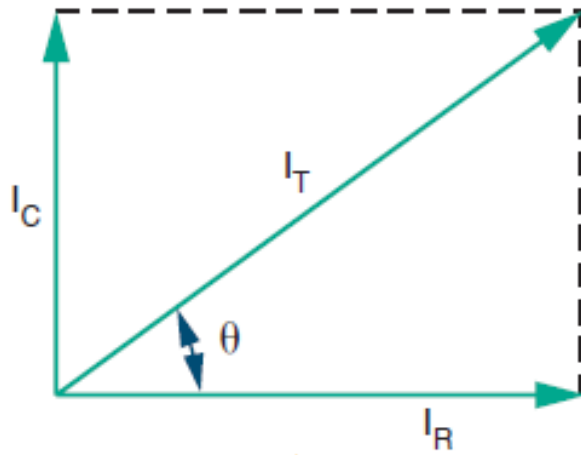

$$I = \sqrt{I_R^2 + I_C^2}$$


$$1/Z = 1/R + 1/X_C \angle -90$$

POWER

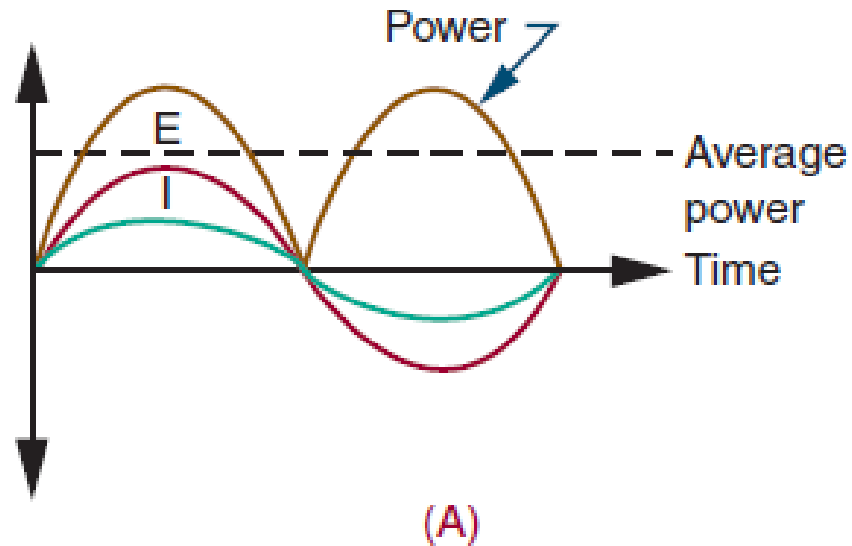


Power Dissipation in a Resistive Circuit has a non-zero value



Power Dissipation in a Reactive Circuit

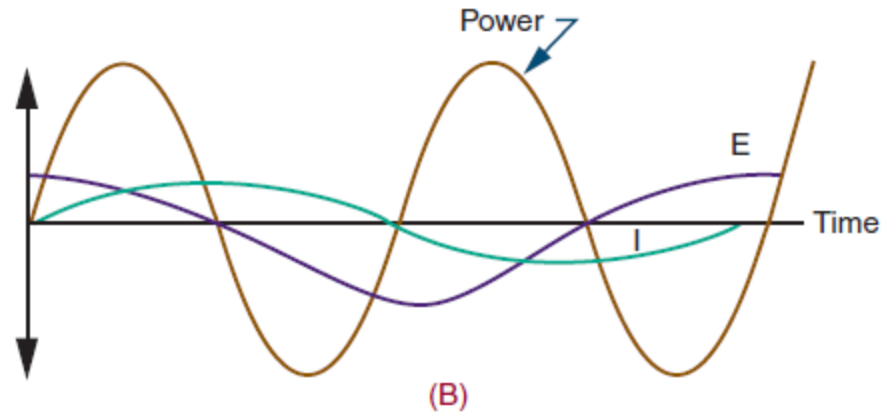

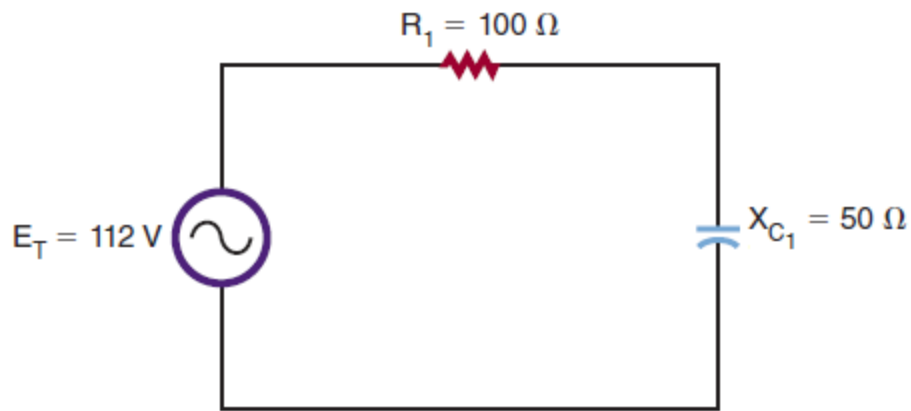In a reactive circuit there is no average or net power loss




Calculate Current

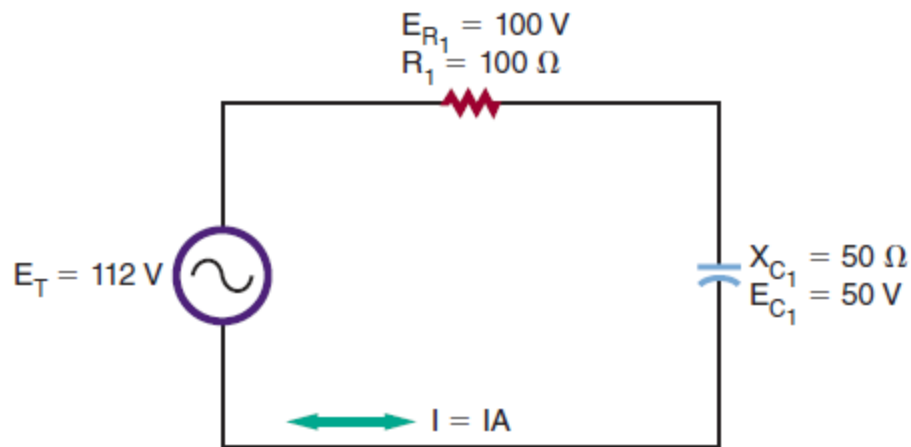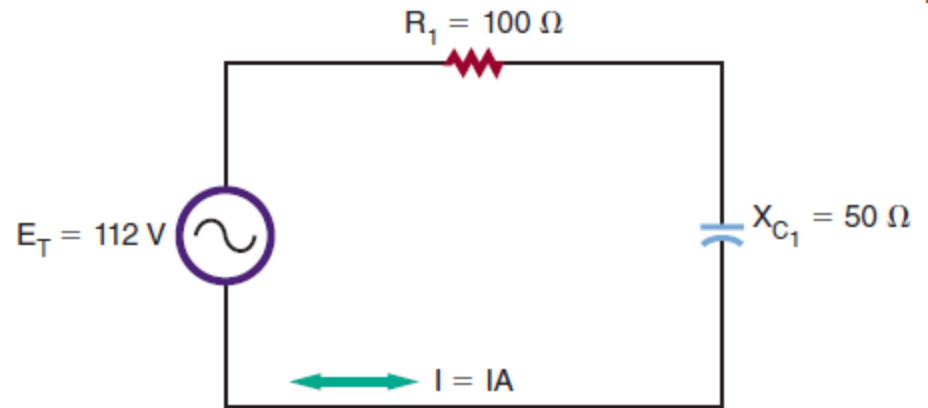

Calculate voltage at each component

Calculate power at each component by VI

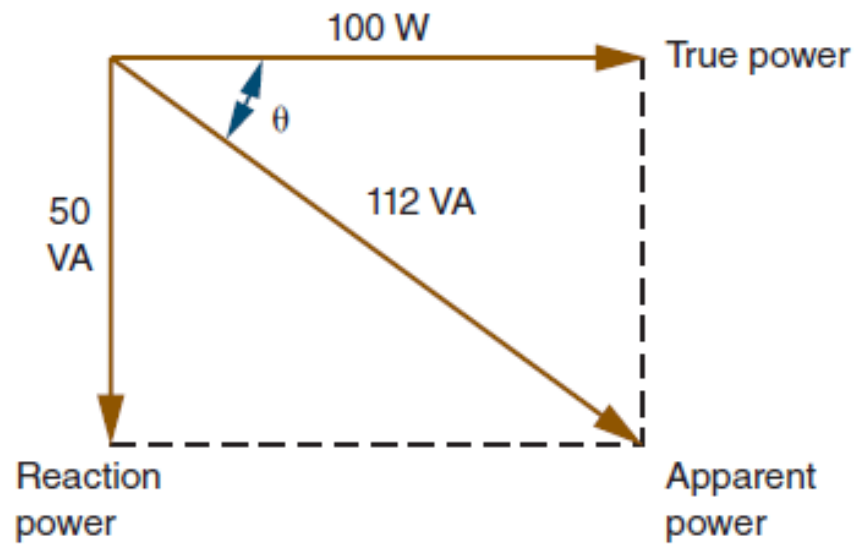

Power Factor= True Power/Apparent Power

Conclusions regarding Power:

- ▶ For pure resistive circuits


Power factor=1

- ▶ For pure inductive circuit

Power factor=0

- ▶ For heavy loads its important consideration that **cables must be capable of handling the apparent power**

INTRODUCTION TO RESONANCE

- ▶ Occurs in many fields and also in ELECTRONICS
 - ▶ Device produces broadening or damping effect at resonance
 - ▶ RADIO and TV RECEIVERS—TUNE at a particular frequency because of resonance.
 - ▶ Tuning Circuit—C parallel L
- 

OVERVIEW FROM PRACTICAL CLASS

- ▶ Parallel tuned ckt— Z_{\max}
- ▶ Condition for Resonance
- ▶ R doesn't effect F_r
- ▶ Resonant Circuits not used in audio bands of frequencies